

Lab 2: Prelab

1) a) $I_s = 10^{-15} \text{ A}$

$I = 10^{-9} \text{ A}$

$U_T = 25 \text{ mV} = 25 \times 10^{-3} \text{ V}$

$\frac{10^{-9} \text{ A}}{10^{-15} \text{ A}} = 10^6$

$I = I_s (e^{\frac{V}{U_T}} - 1)$

$\frac{I}{I_s} = (e^{\frac{V}{U_T}} - 1)$

$10^6 = e^{\frac{V}{25 \times 10^{-3}}} - 1$

This will be a very large number,

on the scale of 10^6 . Therefore the -1 at the end doesn't make much difference. So this would be a good approximationb) Increase current by e

$I = I_s (e^{V_1/U_T})$

$eI = I_s (e^{V_2/U_T})$

$I = I_s (e^{V_2/U_T}) \cdot e^{-1}$

$I = I_s e^{V_1/U_T}$

$I = I_s e^{V_2/U_T - 1}$

Set the I values equal and take natural log

$\frac{V_1}{U_T} = \frac{V_2}{U_T} - 1 \Rightarrow V_1 = V_2 - U_T \Rightarrow \boxed{V_2 = V_1 + U_T}$

↑
with increased current↑
increases by U_T

Increase current by 10 (one decade)

$I = I_s (e^{V_1/U_T})$

$10I = I_s (e^{V_2/U_T})$

$\frac{I}{I_s} = e^{V_1/U_T}$

$10 \cdot \frac{I}{I_s} = e^{V_2/U_T}$

$\ln \frac{I}{I_s} = \frac{V_1}{U_T}$

$\ln 10 + \ln \frac{I}{I_s} = \frac{V_2}{U_T}$

$\ln \frac{I}{I_s} = \frac{V_2}{U_T} - \ln 10$

Set the equations equal

$\frac{V_1}{U_T} = \frac{V_2}{U_T} - \ln 10 \Rightarrow \boxed{V_2 = U_T \ln 10 + V_1}$

↑
New voltage with increased current↑
voltage increases by $U_T \ln 10$

1) c) Incremental diode resistance (dynamic or slope resistance)

$$r_d = \frac{\partial V}{\partial I}$$

$$I = I_s (e^{V/u_T})$$

the -1 would be a constant and would be zero with the derivative anyway.

$$\frac{I}{I_s} = e^{V/u_T}$$

$$\ln \frac{I}{I_s} = \frac{V}{u_T} \Rightarrow \ln I - \ln I_s = \frac{V}{u_T} \Rightarrow u_T (\ln I - \ln I_s) = V$$


$$\frac{\partial V}{\partial I} = u_T \cdot \frac{1}{I} = \boxed{\frac{u_T}{I} = r_d = \frac{\partial V}{\partial I}}$$

d) No, the situation would not differ the relationship between I and V from the ideal diode equation remains the same if you apply a voltage or current.

$$e) I = I_s e^{\frac{V}{u_T}} \Rightarrow \ln I = \ln I_s + \frac{V}{u_T}$$


$$\boxed{\ln I = \underbrace{V \cdot \frac{1}{u_T}}_y + \underbrace{\ln I_s}_b}$$

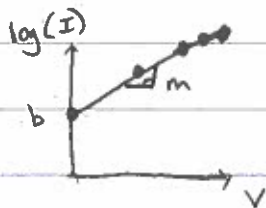with the I - V characteristics, they can be plotted on a semilog scale (semilog for y) and fit with the equation above. The slope of the best fit line would be $\frac{1}{u_T}$ and by looking at the y -intercept we can find I_s .



2)

a)

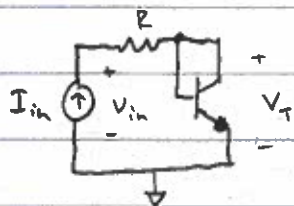

$$I = I_s e^{V/V_T}$$

$$\ln \frac{I}{I_s} = \frac{V}{V_T}$$

$$V_D = V_T \ln \frac{I}{I_s}$$

$$V_{in} - V_D = IR \quad \leftarrow \text{Voltage across } R$$

$$V_{in} - V_T \ln \frac{I}{I_s} = IR$$

$$V_{in} = IR + V_T \ln \frac{I}{I_s} \quad \leftarrow V_{in}$$

$$V_T = V_T \ln \frac{I}{I_s} \quad \leftarrow \text{Voltage across diode}$$

$$V_R = IR \quad \leftarrow \text{Voltage across } R$$

b) $I + \delta I$

Change in
Voltage across
resistor

Change in
Voltage
across
diode

$$\delta V_R = \delta I R$$

$$\delta V_D = \delta I \cdot r_d$$

$$V_{in} = \delta V_R + \delta V_D$$

$$\delta V_{in} = \delta I R + \delta I r_d \Rightarrow \delta V_{in} = \delta I (R + r_d)$$

$$\text{Where } r_d = \frac{V_T}{I}$$

↑
Change in V_{in}

$$c) \Delta IR = \Delta I r_d$$

$$R = \frac{V_T}{I} \Rightarrow \boxed{I_{on} = \frac{V_T}{R}}$$

$$d) I_{on} = I_s e^{V_{on}/V_T} \Rightarrow \ln \left(\frac{I_{on}}{I_s} \right) = \frac{V_{on}}{V_T} \Rightarrow \boxed{V_{on} = V_T \cdot \ln \left(\frac{I_{on}}{I_s} \right)}$$

$$2) \quad e) \quad \frac{\delta V_R}{\delta V_{in}} = \frac{\frac{\delta I R}{\delta I(R+r_d)}}{\delta I(R+r_d)} = \frac{R}{R+r_d}$$

$$= \frac{\frac{U_T}{I_{on}}}{\frac{U_T}{I_{on}} + \frac{U_T}{I}} = \frac{\frac{U_T}{I_{on}}}{\frac{I U_T + I_{on} U_T}{I I_{on}}}$$


$$= \frac{U_T}{I_{on}} \cdot \frac{I I_{on}}{I U_T + I_{on} U_T} = \boxed{\frac{I}{I + I_{on}} = \frac{\delta V_R}{\delta V_{in}}}$$

$$\frac{\delta V_T}{\delta V_{in}} = \frac{\frac{\delta I r_d}{\delta I(R+r_d)}}{\delta I(R+r_d)} = \frac{r_d}{R+r_d} \Rightarrow \frac{\frac{U_T}{I}}{\frac{U_T}{I_{on}} + \frac{U_T}{I}}$$

$$= \frac{\frac{U_T}{I}}{\frac{I U_T + I_{on} U_T}{I I_{on}}} = \frac{U_T}{I} \cdot \frac{I I_{on}}{I U_T + I_{on} U_T} = \boxed{\frac{I_{on}}{I + I_{on}} = \frac{\delta V_T}{\delta V_{in}}}$$

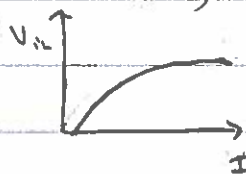
f) $I \ll I_{on}$: $\frac{I_{on}}{0 + I_{on}} = 1 \therefore \delta V_{in}$ is largely contributed by δV_d

V_{in} will change with I following a logarithmic function
 ← this shape




$I \gg I_{on}$: $\frac{I_{on}}{\infty + I_{on}} \approx 0 \therefore \delta V_{in}$ is barely if at all contributed by δV_d

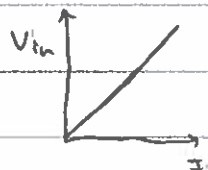Thus, the voltage drop across the transistor at $I \gg I_{on}$ because it is proportional to R with a linear relationship



$$\delta V_{in} \propto R$$

2) g) 'Ideal' diode I-V plot

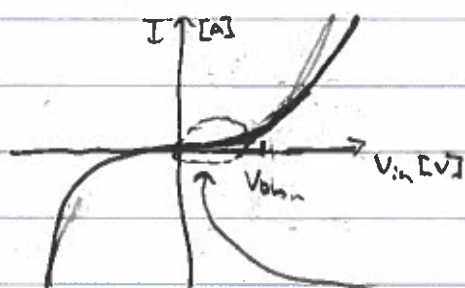


$V_{in} < V_{on}$ by a few U_T

This would be in this region. Therefore, the current will remain close zero and depend very little on V_{in} .

It presumably can be modelled with a linear fit.

$V_{in} > V_{on}$ by a few U_T

This regime would be in this region

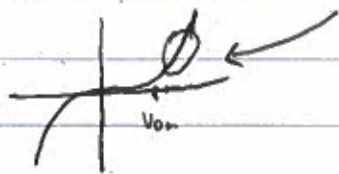

Therefore, the current will depend largely on V_{in} . It will follow an exponential relationship in this region.

